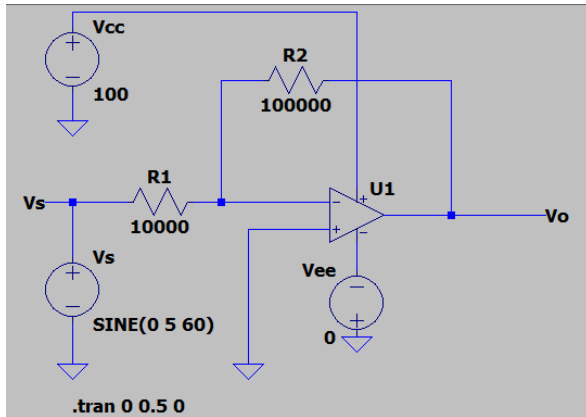


Assignment 1: Basic Circuits with Idealized Op-amp Model

Exercise 1

a.

Schematic:




Netlist:

```
*C:\Users\gurle\OneDrive\Documents\LTspiceXVII\ElecEng 2CF3 assignments.asc
XU1 0 N002 N001 N003 Vo level2
Avol=1Meg GBW=10Meg Slew=10Meg
Ilimit=25m Rail=0 Vos=0 En=0 Enk=0 In=0
Ink=0 Rin=500Meg
Vs Vs 0 SINE(0 5 60)
Vee 0 N003 0
Vcc N001 0 100
R1 N002 Vs 10000
R2 Vo N002 100000
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

b.

Plot:

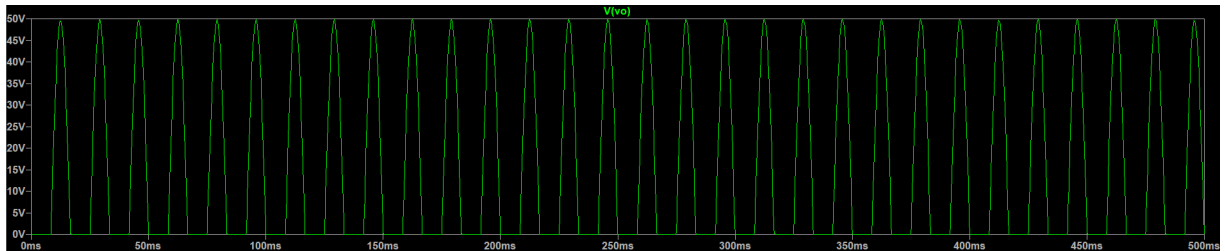

Netlist:

```
*C:\Users\gurle\OneDrive\Documents\LTspiceXVII\ElecEng 2CF3 assignments.asc
XU1 0 N002 N001 N003 Vo level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vs Vs 0 SINE(0 5 60)
Vee 0 N003 0
Vcc N001 0 100
R1 N002 Vs 10000
R2 Vo N002 100000
.tran 0 0.5 0
```


```
.lib UniversalOpAmp2.lib
.backanno
.end
```

Explain the behavior of V_0 . Which half-periods of V_s (the positive or the negative) are amplified and transferred to the output and which are cut out?

V_0 has a maximum of about 50V and is constantly oscillating, but when it reaches 0V, it stays constant until the voltage is bigger than 0V again. The negative half-periods of V_s are amplified and transferred to the output and the positive half-periods of V_s are cut out because the inverting op-amp is being used.

c.

Plot:

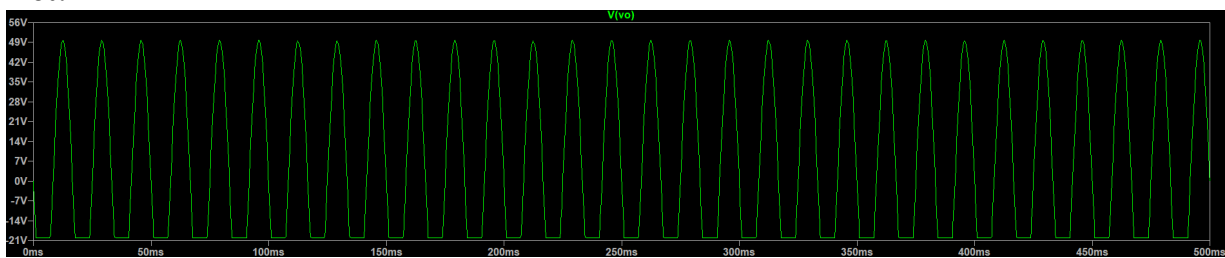


Netlist:

```
* C:\Users\gurle\OneDrive\Documents\LTspiceXVII\ElecEng 2CF3 assignments.asc
XU1 0 N002 N001 N003 Vo level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vs Vs 0 SINE(0 5 60)
Vee 0 N003 20
Vcc N001 0 100
R1 N002 Vs 10000
R2 Vo N002 100000
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

Explain the behavior of V_0 . Which values within the V_s waveform are amplified and transferred to the output and which are cut out?


V_0 has a maximum of about 50V and is constantly oscillating, but when it reaches -21V, it stays constant until the voltage is bigger than -21V again. Values above -21V are amplified and transferred out, while values below -21V are cut out.


d.

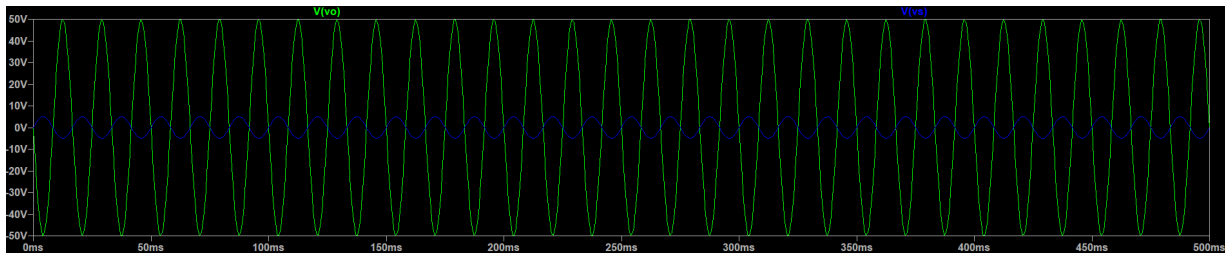Plot:**Netlist:**

```
* C:\Users\gurle\OneDrive\Documents\LTspiceXVII\ElecEng 2CF3 assignments.asc
XU1 0 N002 N001 N003 Vo level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vs Vs 0 SINE(0 5 60)
Vee 0 N003 100
Vcc N001 0 100
R1 N002 Vs 10000
R2 Vo N002 100000
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

e.

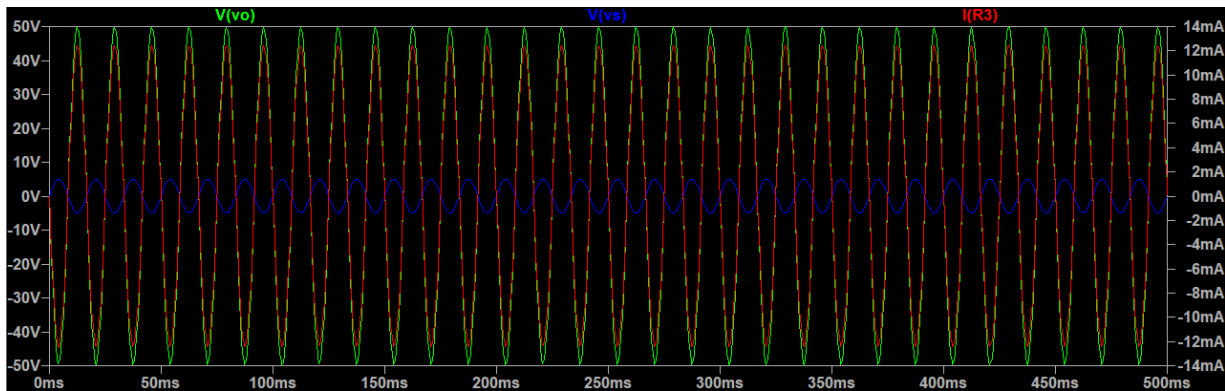Plot 1:**Plot 2:**

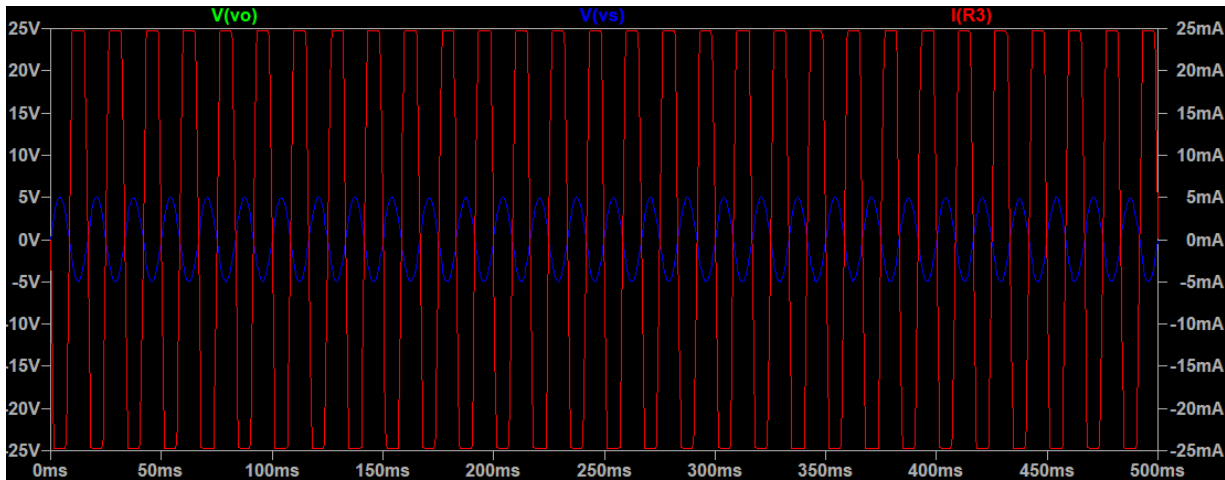**Netlist:**

```
* C:\Users\gurle\OneDrive\Documents\LTspiceXVII\ElecEng 2CF3 assignments.asc
XU1 0 N002 N001 N003 Vo level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vs Vs 0 SINE(0 5 60)
Vee 0 N003 100
Vcc N001 0 100
R1 N002 Vs 10000
R2 Vo N002 100000
R3 Vo 0 1000
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

What is the value of $R_{L,min}$? $R_{L,min} = V_{0,max} / I_{0,max} = 2000\Omega$


What is the observed maximum value of V_0 with $R_L = 2 R_{L,min}$ and what is it with $R_L = 0.5 R_{L,min}$? Is there a difference? Explain why you observe these values referring also to the observed maximum values of I_0 in both cases.

The observed maximum value of V_0 with both R_L s are both 100V.

Exercise 2

- a. *assuming R_I = sum of last 2 digits of student #*

Schematic:

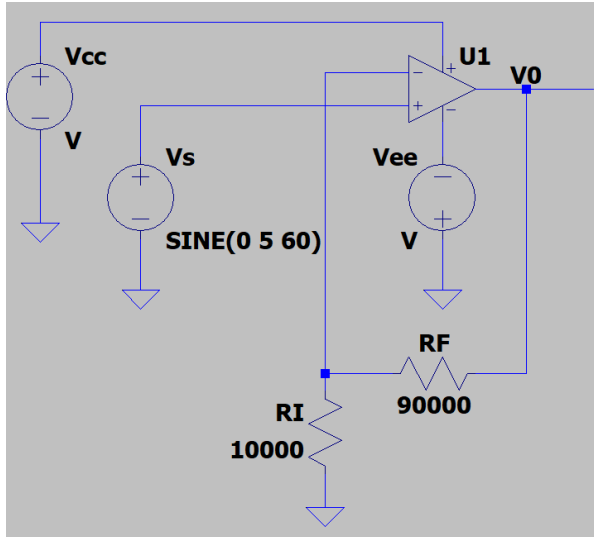


Netlist:

```
*C:\Users\gurle\OneDrive\Documents\LTspiceXVII\eleceng 2cf3
assignments\assig1_q2.asc
RI 0 N002 10000
RF N002 V0 90000
Vcc N001 0 V
Vee 0 N004 V
Vs N003 0 SINE(0 5 60)
XU1 N003 N002 N001 N004 V0 level2
Avol=1Meg GBW=10Meg Slew=10Meg
Ilimit=25m Rail=0 Vos=0 En=0 Enk=0 In=0
Ink=0 Rin=500Meg
.lib UniversalOpAmp2.lib
.backanno
.end
```

- b.

Plot:

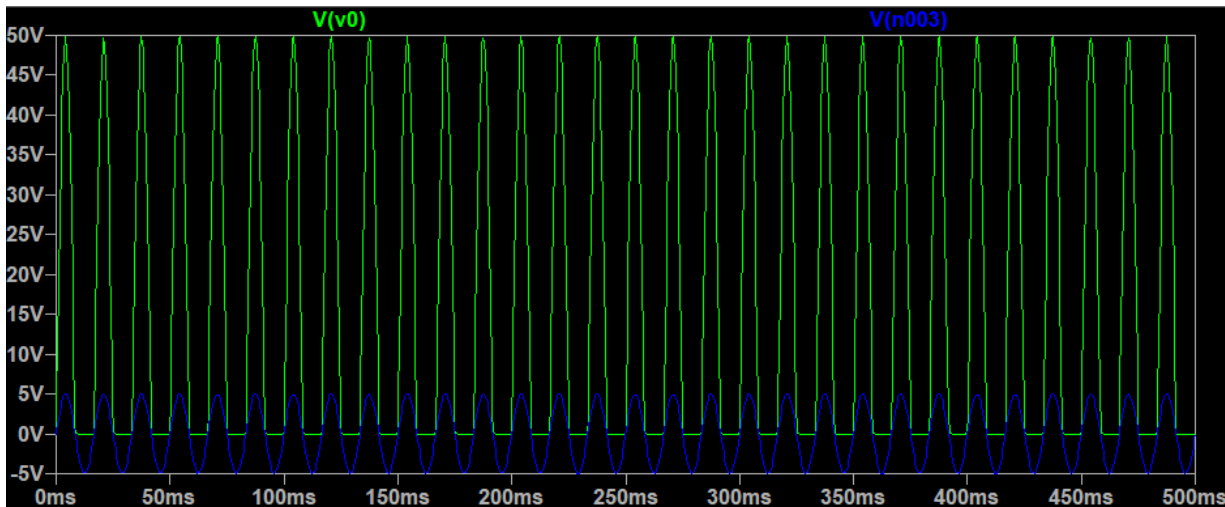

Netlist:

```
* C:\Users\gurle\OneDrive\Documents\LTspiceXVII\eleceng 2cf3 assignments\assig1_q2.asc
RI 0 N002 10000
RF N002 V0 90000
Vcc N001 0 100
Vee 0 N004 0
Vs N003 0 SINE(0 5 60)
```

```
XU1 N003 N002 N001 N004 V0 level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

Has your circuit achieved the desired gain of 10?


The desired gain has been achieved because the V₀ output has a peak 10x larger than the peak of V_s.

Is it operating in a non linear regime? Justify your answer.

It is not operating in a non-linear regime because the V₀ value is within the V_{ee} and V_{cc} values.

c.

Plot:

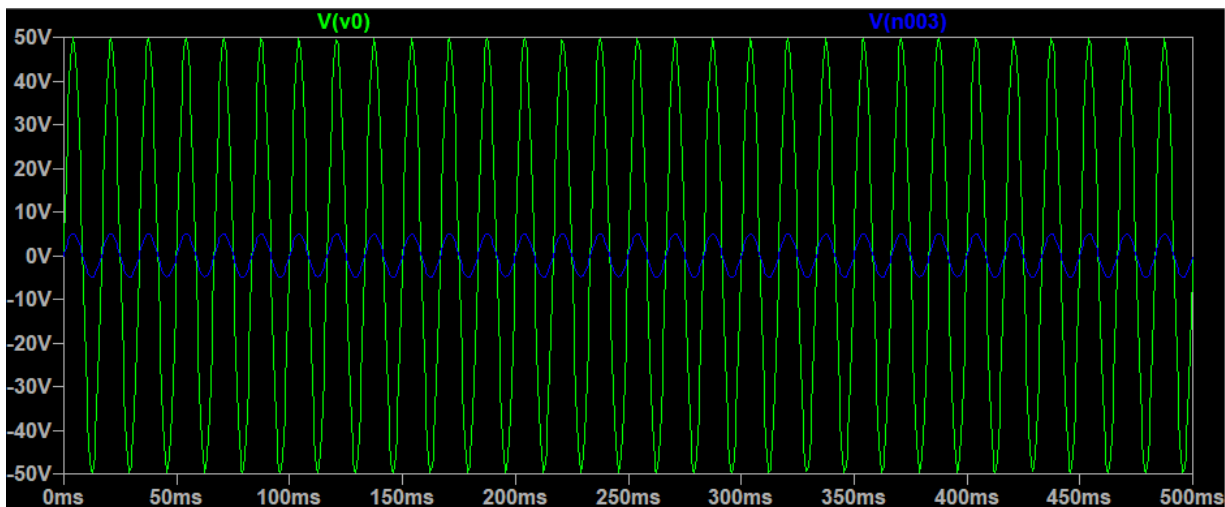

Netlist:

```
* C:\Users\gurle\OneDrive\Documents\LTspiceXVII\eleceng 2cf3 assignments\assig1_q2.asc
RI 0 N002 10000
RF N002 V0 90000
Vcc N001 0 100
Vee 0 N004 100
Vs N003 0 SINE(0 5 60)
XU1 N003 N002 N001 N004 V0 level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
```

.end

Has your circuit achieved the desired gain of 10?


The desired gain has been achieved because the V_0 output has a peak 10x larger than the peak of V_s .

Is it operating in a linear regime? Justify your answer.

It is operating in a linear regime because the V_0 value is within the V_{ee} and V_{cc} values.

d.


Plot 1:

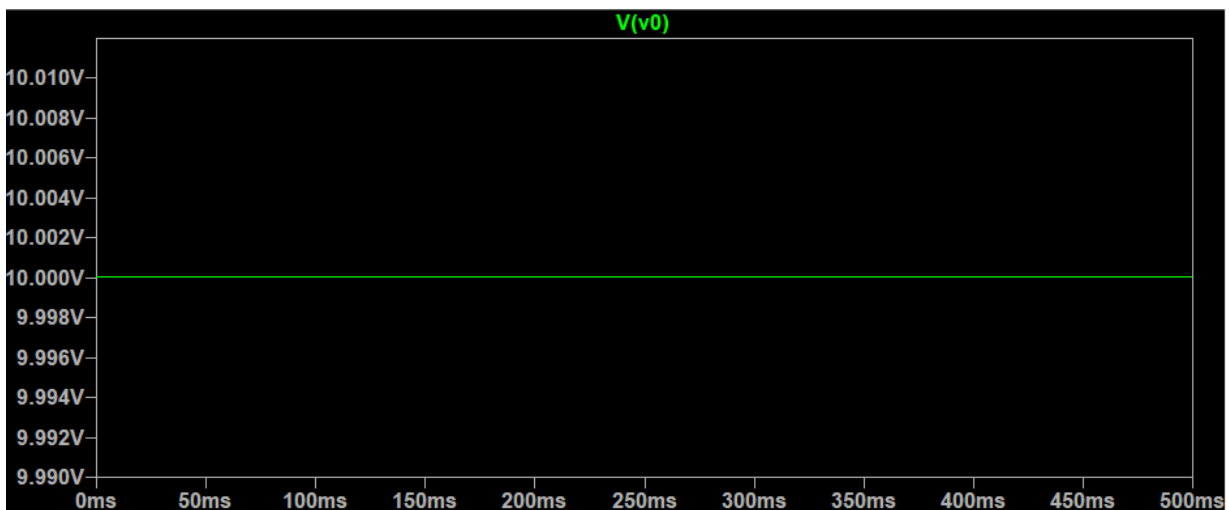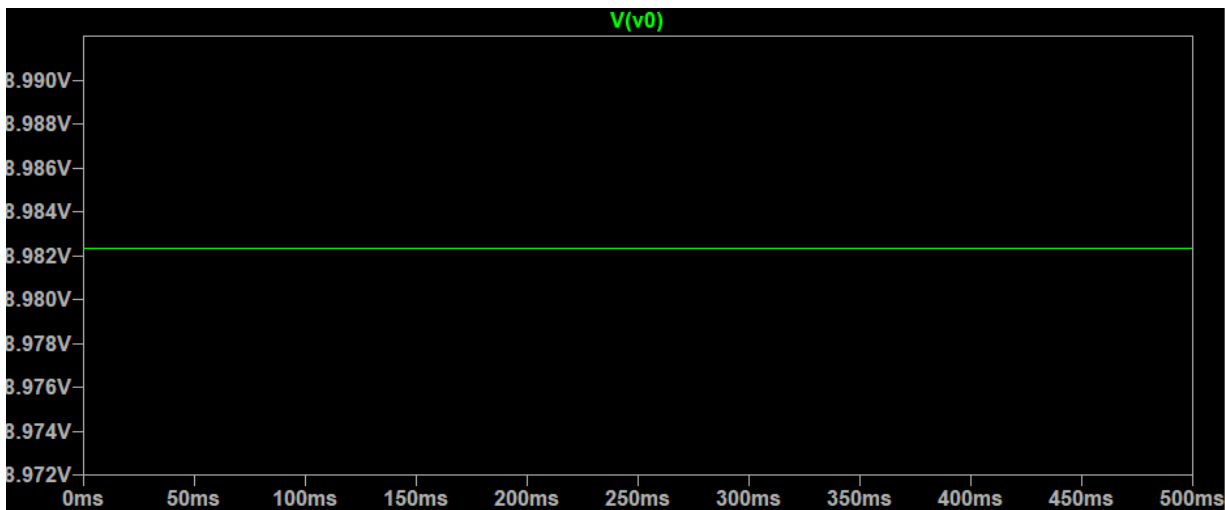

Netlist 1:

```
* C:\Users\gurle\OneDrive\Documents\LTspiceXVII\eleceng 2cf3 assignments\assig1_q2.asc
RI 0 N002 10000
RF N002 V0 90000
Vcc N001 0 100
Vee 0 N004 100
Vs N003 0 1
XU1 N003 N002 N001 N004 V0 level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

Plot 2:

**Netlist 2:**

```
* C:\Users\gurle\OneDrive\Documents\LTspiceXVII\eleceng 2cf3 assignments\assig1_q2.asc
RI 0 N002 10000
RF N002 V0 90000
Vcc N001 0 100
Vee 0 N004 100
Vs N003 0 1
XU1 N003 N002 N001 N004 V0 level2 Avol=100 GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

What is the circuit gain in the case when $A_{ol} = 100$? ~8.982V

What is the gain error in percentage compared to the ideal gain of 10?

$$\text{gain error} = 100\% * (\text{actual} - \text{ideal})/\text{ideal} = -10.18\%$$